
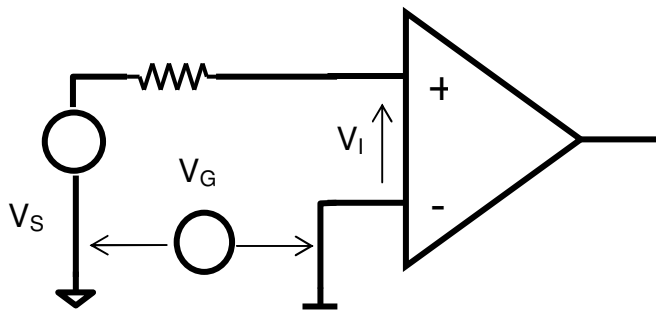


AMPLIFICADORES

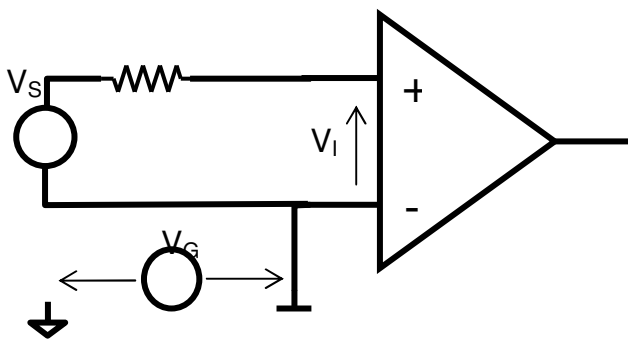



$$V_I = V_S + V_G$$

$$\left(\frac{S}{N}\right)_I = \frac{V_{IS}}{V_{IG}} = \frac{V_S}{V_G}$$



$$V_{IS} = V_S$$



$$V_G = 0$$

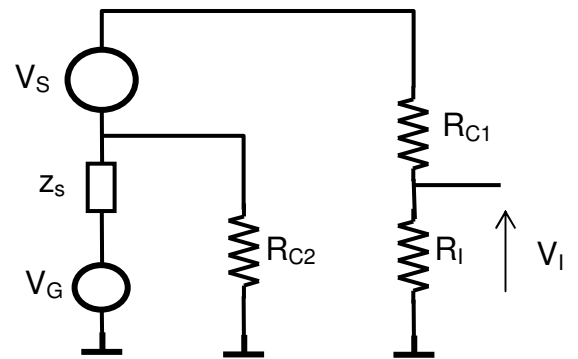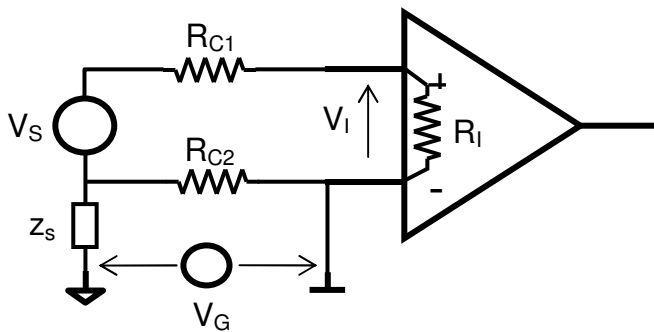


$$V_{IS} = V_S \cdot \frac{R_I}{(Z_S // R_{C2}) + R_{C1} + R_I}$$

$$V_{IG} = V_G' \cdot \frac{R_I}{(Z_S // R_{C2}) + R_{C1} + R_I}$$
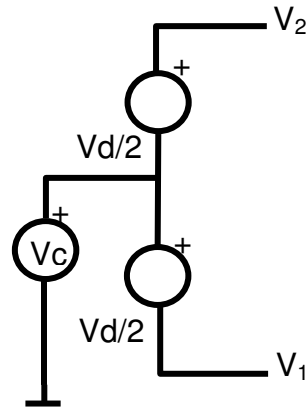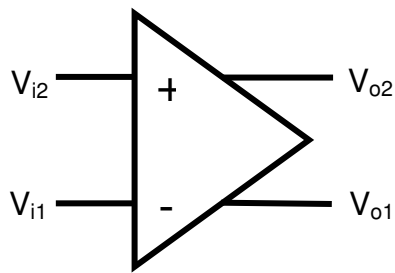
$$V_G' = V_G \cdot \frac{R_{C2}}{R_{C2} + Z_S}$$


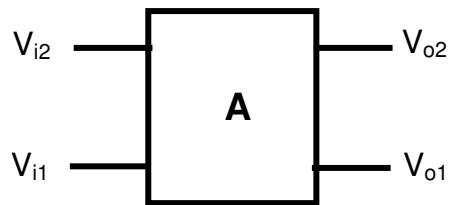
$$V_d = V_2 - V_1 \quad ; \quad V_c = \frac{V_2 + V_1}{2}$$



$$V_{od} = A_{DD} \cdot V_{id} + A_{DC} \cdot V_{ic}$$

$$V_{oc} = A_{CD} \cdot V_{id} + A_{CC} \cdot V_{ic}$$

$$CMRR = \frac{A_{DD}}{A_{DC}}$$


$$E = \frac{A_{CD}}{A_{DD}}$$

$$V_{od} = A_{DD} \left(V_{id} + \frac{V_{ic}}{CMRR} \right)$$

EN UN AMPLIFICADOR "SINGLE ENDED" ($V_{o1} = 0$) SOLO ESTÁN DEFINIDAS A_{DD} Y A_{DC} .


$$V_0 = A_D \cdot V_{id} + A_C \cdot V_{ic}$$

AMPLIFICADORES DE INSTRUMENTACIÓN

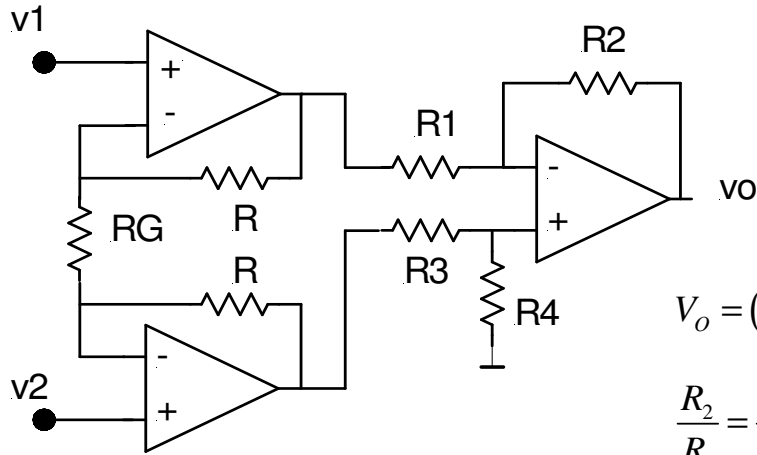


$$V_o = (V_2 - V_1) \left(\frac{R_2}{R_1} \right) \left(\frac{2R}{R_G} + 1 \right)$$

$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$

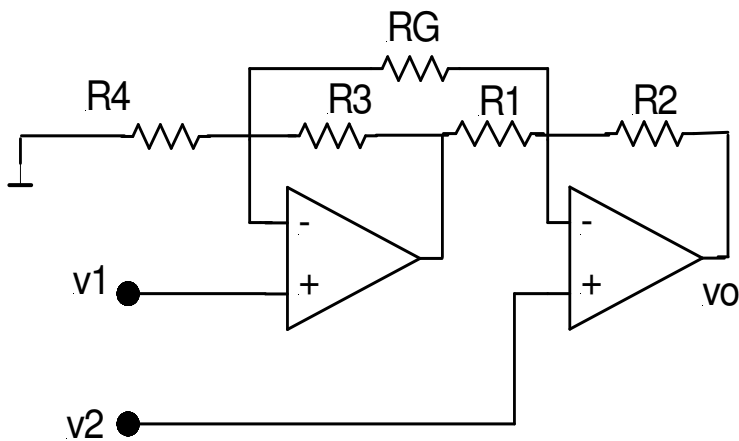

$$V_o = (V_2 - V_1) \left(1 + \frac{R_2}{R_1} + 2 \frac{R_2}{R_G} \right)$$


$$R_1 = R_3 ; R_2 = R_4$$

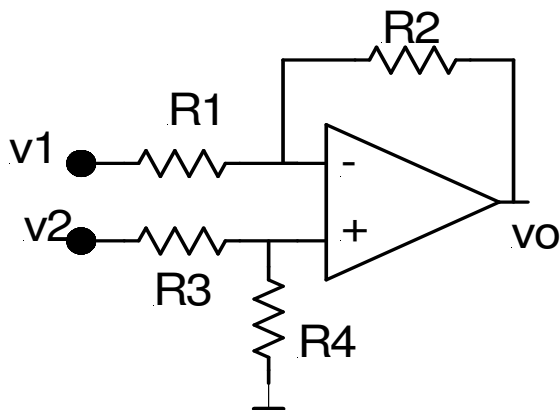

$$V_o = (V_2 - V_1) \cdot \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} \quad (0,1\% \Rightarrow \text{CMRR} \leq 66 \text{ db})$$

EJEMPLO: PUENTES DE MEDIDA

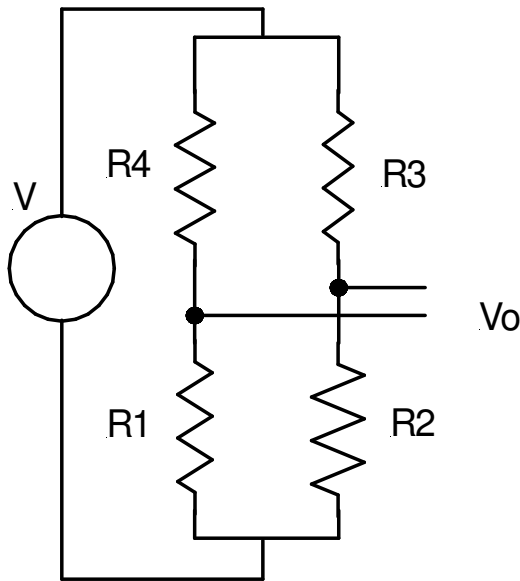

$$V_o = \left(\frac{R2}{R2 + R3} - \frac{R1}{R1 + R4} \right) V =$$

$$= \frac{\frac{R4}{R1} - \frac{R3}{R2}}{\left(1 + \frac{R4}{R1} \right) \left(1 + \frac{R3}{R2} \right)} V$$

Si $\frac{R4}{R1} = \frac{R3}{R2}$ $V_o = 0$

Si $R1 = R2 = R4 = R$ (un solo elemento variable)
y $R3 = R(1 + \delta)$

$$V_o = \frac{\delta V}{2(2 + \delta)}$$



Si $R2 = R4 = R$
y $R1 = R3 = R(1 + \delta)$ (mayor sensibilidad)

$$V_o = \frac{1 - (1 + \delta)^2}{(2 + \delta)^2} V \cong \frac{2\delta}{\delta + 1} V$$

Si $R1 = R4 = R$
y $R2 = R(1 + \delta)$
 $R3 = R(1 - \delta)$

$$V_o = \frac{\delta}{2} V$$

CIRCUITO EQUIVALENTE.

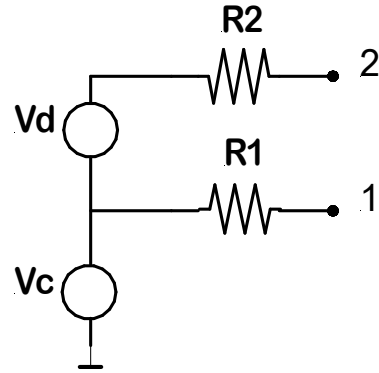
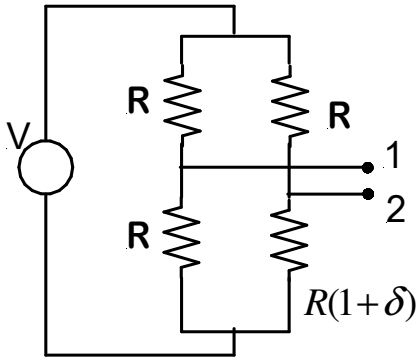


$$V_d = \frac{V}{2} \frac{\delta}{(2 + \delta)}$$

$$R_1 = \frac{R}{2}$$

$$V_c = \frac{V}{2}$$
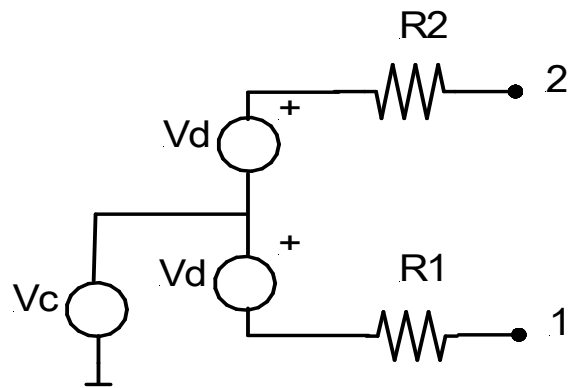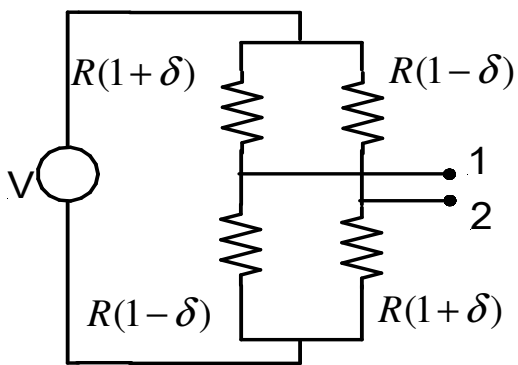
$$R_2 = R \frac{1 + \delta}{1 - \delta}$$



$$V_d = \frac{V}{2} \delta$$

$$R_1 = R_2 = \frac{(1 - \delta^2)}{2}$$

$$V_c = \frac{V}{2}$$

GUARDAS

